



CSE260: Digital Logic Design
Summer 2025
Quiz - 02
Duration: 25 minutes

A

Name: <u>Solution</u>	ID:	Section:
-----------------------	-----	----------

1.CO2	Convert the Boolean function to its Canonical SOP form. $F(A,B,C) = (B'+C)' \cdot (AC+B) + A'$	5
2.CO2	$F(A,B,C,D) = \Sigma(0,1,2,5,6,7,8,9,10,13)$ a. Use Karnaugh Map to find the simplified expression. b. Implement the simplified expression using only NAND gates	10

$$1) F = (B'+C)' \cdot (AC+B) + A'$$

$$= B \cdot C' \cdot (AC+B) + A'$$

$$= ABC \cdot C' + BC' + A'$$

$$= BC' + A'$$


$$= BC'(A+A') + A'(B+B')(C+C')$$

$$= ABC' + A'BC' + (A'B + A'B')(C+C')$$

$$= ABC' + A'BC' + A'B'C + A'BC' + AB'C + AB'C'$$

$$= 110, 010, 011, 100, 101, 100$$

$$= \Sigma(6, 2, 3, 5, 4)$$

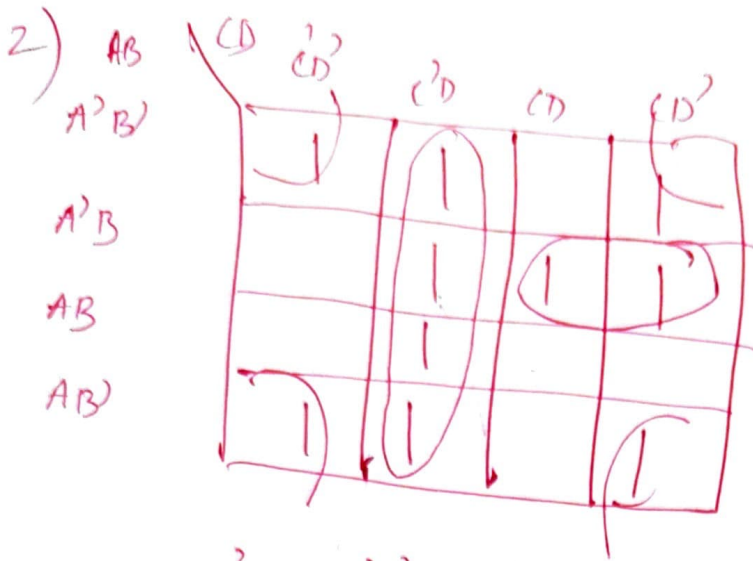

$$F = C'D + B'D' + A'BC$$

A B C D

