

Name: <u>Solution</u>	ID:	Section:
-----------------------	-----	----------

1.CO1	Convert the Boolean function to its Canonical SOP form. $F(X,Y,Z) = (Y'+Z)' \cdot (XZ+Y) + X'$	5
2.CO1	$F(A,B,C,D) = \Sigma(0,1,3,4,5,8,9,11)$ c. Use Karnaugh Map to find the simplified expression. d. Implement the simplified expression using only NOR gates	10

$$F = y \cdot z' \cdot (xz + y) + x'$$

$$= \underline{xyz \cdot z'} + yz' + x'$$

$$= yz' + x'$$

$$= yz'(x+x') + x'(y+y')(z+z')$$


$$= xyz' + x'yz' + (x'y + xy')(z+z')$$

$$= xyz' + x'yz' + x'y z + x'y z' + xy'z + xy'z'$$

$$= 110, 010, 011, 010, 101, 100$$

$$= \Sigma(6, 2, 3, 5, 4)$$

2) F

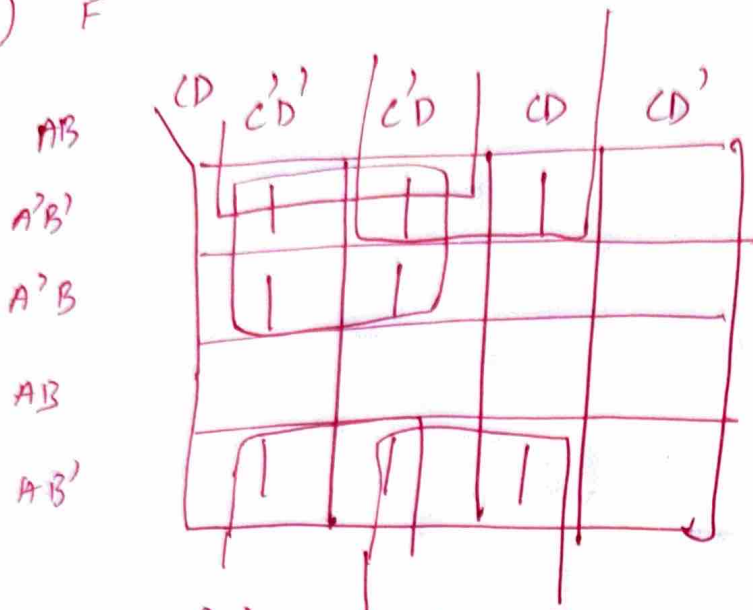

$$F = A'C' + B'C' + B'D$$

