

**Question 1 [7 Marks]:**

Simplify the following expression using **tabulation** method ONLY:  $F(A,B,C) = A'B'C' + A'B'C + AB'C + ABC' + ABC$

**Question 2 [8 Marks]:**

Design a circuit diagram for the following comparator system that takes three 3-bit binary numbers [A, B and C] as inputs and outputs in the following fashion:

Output=1; if  $A > 2B$

Output=0; otherwise

NB1: You need to show a gate level diagram for the comparator, meaning you cannot use block diagram of magnitude comparator. However, you may use block diagrams of any other ICs you require.

NB2: Drawing the circuit diagram horizontally in your script may help you.

NB3: You cannot change the equation. You must draw the circuit for the given equation.

**Question 3 [5 Marks]:**

Construct the circuit of the following function using 3:8 decoder and 2:4 decoder only:

$$F(A,B,C,D) = (A+B')(C'+D')$$

NB: You must use both the decoders in a single circuit. Your circuit should be cost efficient, meaning you have to use the lowest number of components possible. You should use external gates for connecting inputs/outputs if required.

**Question 4 [10 Marks]:**

Consider the following sequential circuit. Determine its state table and state diagram.

